



SpinalHDL

An alternative to standard HDL

Summary


- Language introduction / flow
- Simple examples
- Advanced examples
- Meta-hardware description examples

Language introduction

- Open source , started in december 2014
- Focus on RTL description
- Thinked to be interoperable with existing tools
 - It generate VHDL/Verilog files
 - It can integrate VHDL/Verilog IP as blackbox
- Abstraction level :
 - You can design things similary to VHDL/Verilog
 - If you want to, you can use many abstraction utils and also define new ones

Language flow

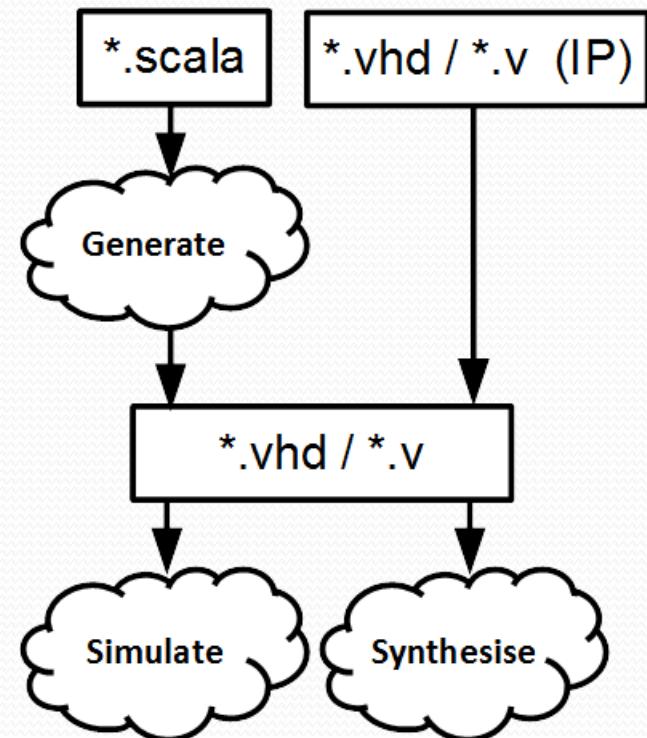
1. Describe your RTL
2. Generate the VHDL/Verilog
3. Simulate and synthesize



Some points about Spinal

- There is no logic overhead in the generated code. (I swear !)
- Spinal HDL is a RTL language. But the generated VHDL/Verilog is simulatable with all standards EDA tools.
- The component hierarchy and all names are preserved during the VHDL/Verilog generation.

Simple examples

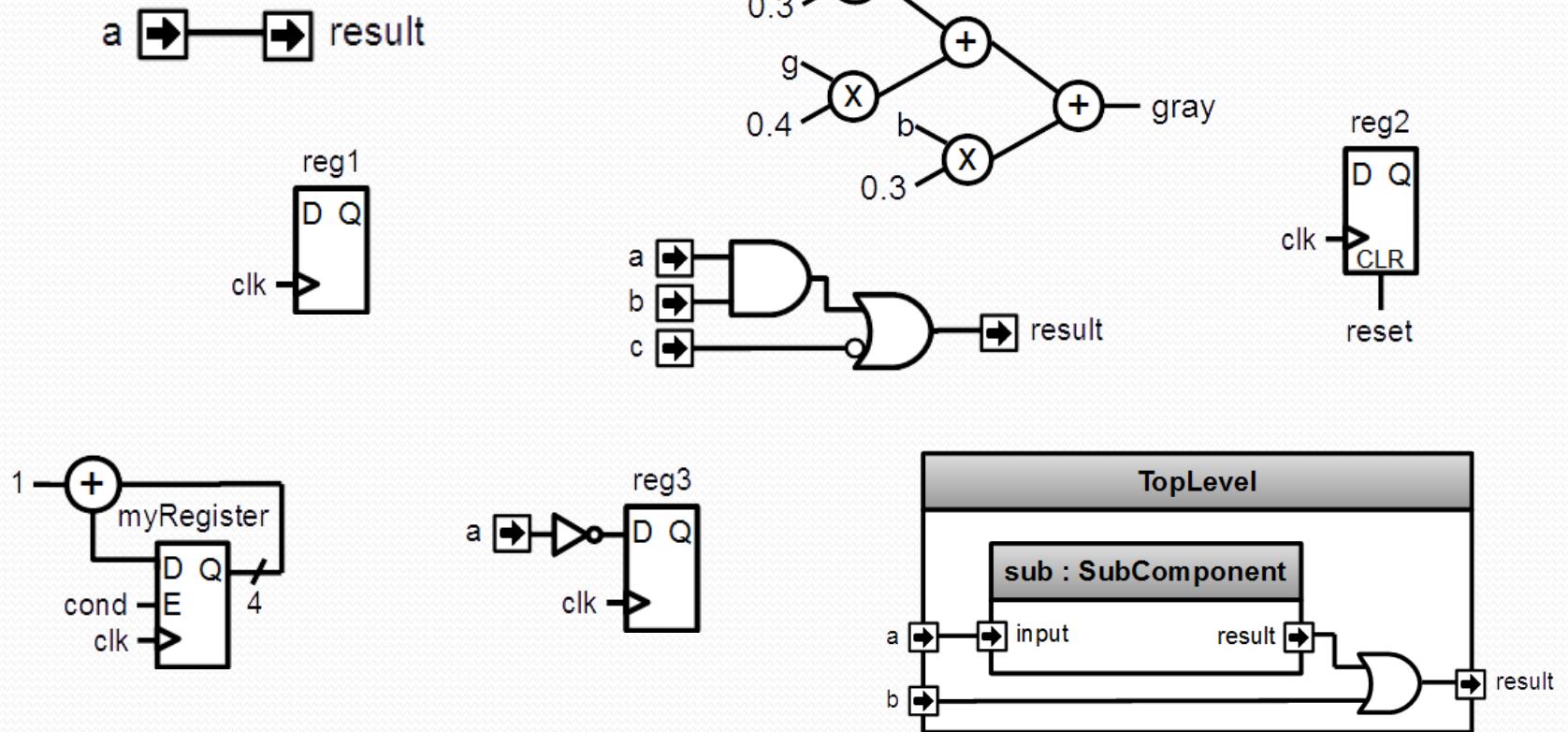

A simple component

```
class MyComponent extends Component {  
    val io = new Bundle {  
        val a      = in  Bool  
        val result = out Bool  
    }  
  
    io.result := io.a  →  a → result  
}
```


Combinatorial logic

```
class MyComponent extends Component {  
    val io = new Bundle {  
        val a      = in  Bool  
        val b      = in  Bool  
        val c      = in  Bool  
        val result = out Bool  
    }  
  
    io.result := (io.a & io.b) | (!io.c)  
}
```



Signals

```
class MyComponent extends Component {  
    val io = new Bundle {  
        val a      = in Bool  
        val b      = in Bool  
        val c      = in Bool  
        val result = out Bool  
    }  
    val a_and_b = Bool  
    a_and_b := io.a & io.b  
  
    val not_c = ! io.c  
  
    io.result := a_and_b | not_c  
}
```

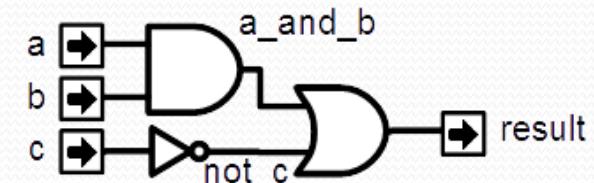

Generated VHDL


```
class MyComponent extends Component {  
    val io = new Bundle {  
        val a      = in  Bool  
        val b      = in  Bool  
        val c      = in  Bool  
        val result = out Bool  
    }  
    val a_and_b = io.a & io.b  
    val not_c = !io.c  
    io.result := a_and_b | not_c  
}
```



```
entity MyComponent is  
    port(  
        io_a : in std_logic;  
        io_b : in std_logic;  
        io_c : in std_logic;  
        io_result : out std_logic  
    );  
end MyComponent;  
  
architecture arch of MyComponent is  
    signal a_and_b : std_logic;  
    signal not_c : std_logic;  
begin  
    io_result <= (a_and_b or not_c);  
    a_and_b <= (io_a and io_b);  
    not_c <= (not io_c);  
end arch;
```

Registers

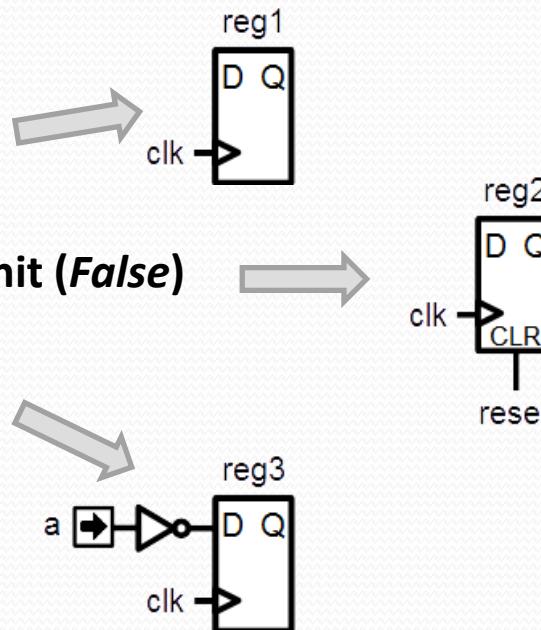
```
class MyComponent extends Component {  
    val io = new Bundle {  
        val a = in Bool  
    }  
  
    val reg1 = Reg(Bool)  
  
    val reg2 = Reg(Bool) init (False)  
  
    val reg3 = Reg(Bool)  
    reg3 := ! io.a  
}
```



No more Process/Always blocks


```
val cond          = Bool  
val mySignal     = Bool  
val myRegister   = Reg(UInt(4 bits))  
val myRegisterWithReset = Reg(UInt(4 bits)) init (0)
```
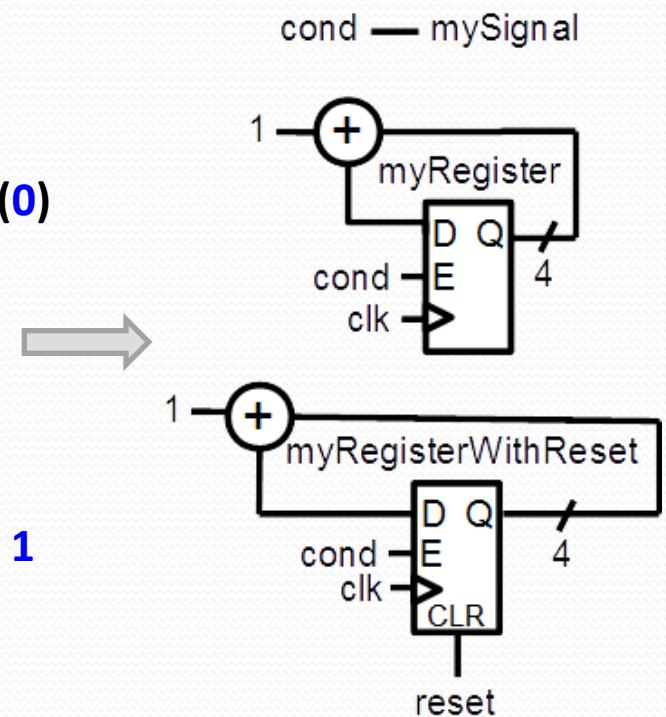
```
mySignal := False  
when(cond) {  
    mySignal      := True  
    myRegister    := myRegister + 1  
    myRegisterWithReset := myRegisterWithReset + 1  
}
```



Component internal organisation
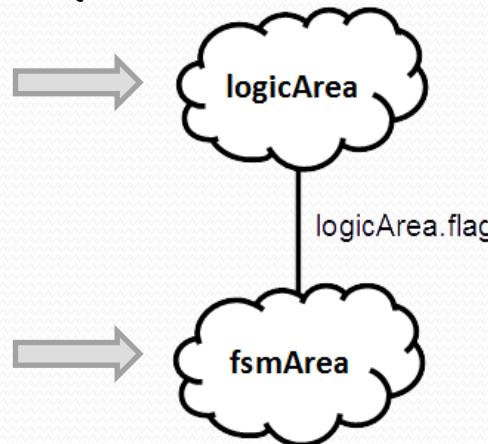
```
class TopLevel extends Component {  
    //...  
    val logicArea = new Area {  
        val flag = Bool  
    }  
  
    val fsmArea = new Area {  
        when(logicArea.flag){  
            //...  
        }  
    }  
}
```




Component instance

```
class SubComponent extends Component{  
    val io = new Bundle {  
        val input = in Bool  
        val result = out Bool  
    }  
    ...  
}
```

```
class TopLevel extends Component {  
    val io = new Bundle {  
        val a = in Bool  
        val b = in Bool  
        val result = out Bool  
    }  
}
```

```
val sub = new SubComponent
```

```
sub.io.input := io.a  
io.result := sub.io.result | io.b  
}
```

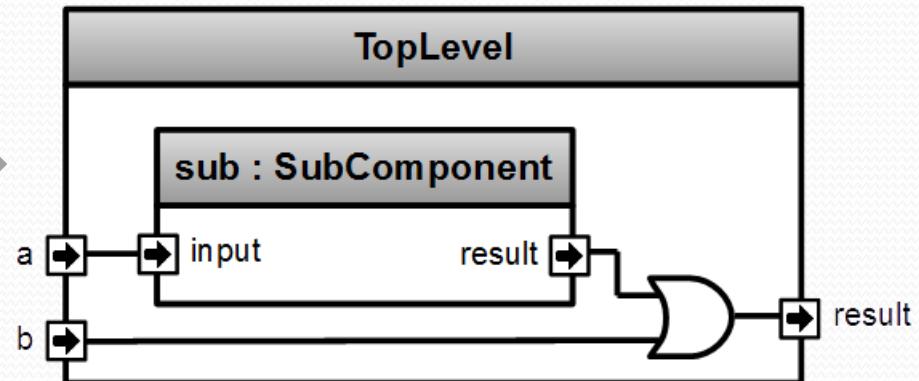

UInt, Vec, When

```
class MyComponent extends Component
{
    val io = new Bundle {
        valconds = in Vec(Bool,2)
        valresult = out UInt(4 bits)
    }

    when(io.conds(0)){
        io.result := 2
    when(io.conds(1)){
        io.result := 1
    }
} otherwise {
    io.result := 0
}
}
```



Enum, Switch

```
object MyEnum extends SpinalEnum {
    val state0, state1 = newElement()
}

class MyComponent extends Component {
    val state = Reg(MyEnum) init(MyEnum.state0)

    switch(state) {
        is(MyEnum.state0) {

        }
        is(MyEnum.state1) {


        }
        default{
            }
    }
}
```

For, Variable, Generics

```
class CarryAdder(size: Int) extends Component {  
    val io = new Bundle {  
        val a      = in UInt (size bits)  
        val b      = in UInt (size bits)  
        val result = out UInt (size bits)  
    }  
  
    var c = False  
    for (i <- 0 until size) {  
        val x = io.a(i)  
        val y = io.b(i)  
  
        io.result(i) := x ^ y ^ c  
        c |= (x & y) | (x & c) | (y & c);  
    }  
}
```

Latch/Loop

```
class MyComponent extends Component {  
    val io = new Bundle {  
        val a      = in  Bool  
        val result = out Bool  
    }  
    //Latch/Loop detected => Error message will come from Spinal  
    io.result := io.a | io.result  
}
```

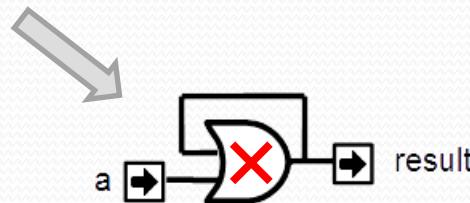

ClockDomains

```
class MyTopLevel extends Component {
    val io = new Bundle {
        val coreClk = in Bool
        val coreReset = in Bool
    }

    val coreClockDomain = ClockDomain(
        clock = io.coreClk,
        reset = io.coreReset,
        config = ClockDomainConfig(
            clockEdge      = RISING,
            resetKind     = ASYNC,
            resetActiveLevel = HIGH
        )
    )

    val coreArea = new ClockingArea(coreClockDomain) {
        val myCoreClockedRegister = Reg(UInt(4 bit))
        //...
    }
}
```

myCoreClockedRegister

The diagram illustrates a D flip-flop register. It features a rectangular box with two output terminals labeled 'D' and 'Q'. A third terminal, labeled 'CLR', is shown with a feedback connection that loops back to the 'D' input. An arrow points from the text 'myCoreClockedRegister' to the 'coreClk' input of the register.

Memory


```
//Memory of 1024 Bool  
val syncRam = Mem(Bool, 1024)  
val asyncRam = Mem(Bool, 1024)  
  
//Write them  
syncRam(5) := True  
asyncRam(5) := True  
  
//Read them  
val syncRam = mem.readSync(6)  
val asyncRam = mem.readAsync(4)
```

Function

```
// Input RGB color  
val r,g,b = UInt(8 bits)
```

```
// Define a function to multiply a UInt by a scala Float value.  
def coefMul(value : UInt,by : Float) : UInt = (value * U((255*by).toInt,8 bits) >> 8)
```
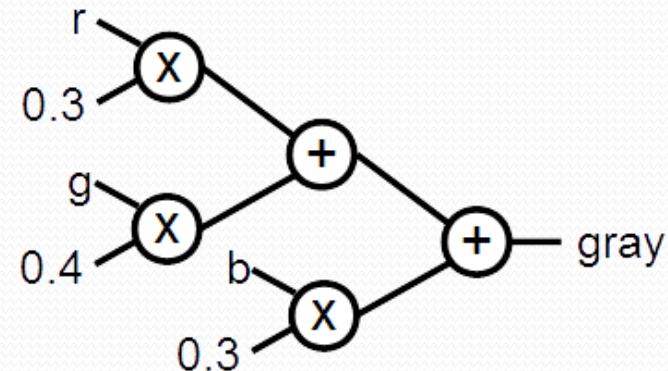
```
//Calculate the gray level  
val gray = coefMul(r, 0.3f) +  
           coefMul(g, 0.4f) +  
           coefMul(b, 0.3f)
```




Function, User utils (1)

```
case class Color(channelWidth: Int) extends Bundle {  
    val r = UInt(channelWidth bit)  
    val g = UInt(channelWidth bit)  
    val b = UInt(channelWidth bit)  
  
    def +(that: Color): Color = {  
        val result = Color(channelWidth)  
  
        result.r := this.r + that.r  
        result.g := this.g + that.g  
        result.b := this.b + that.b  
  
        return result  
    }  
}
```




Function, User utils (2)

```
class ColorSumming(sourceCount: Int, channelWidth: Int) extends Component {  
    val io = new Bundle {  
        val sources = in Vec(Color(channelWidth), sourceCount)  
        val result = out(Color(channelWidth))  
    }  
}
```
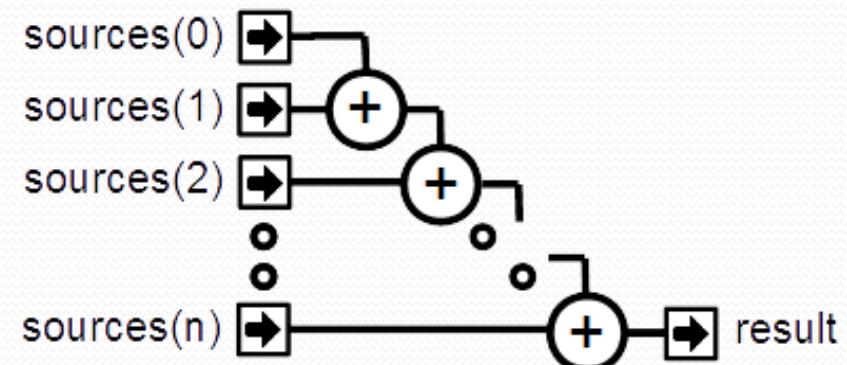
```
var sum = io.sources(0)  
for (i <- 1 until sourceCount) {  
    sum += sum + io.sources(i)  →  
}  
io.result := sum  
}
```



Advanced examples

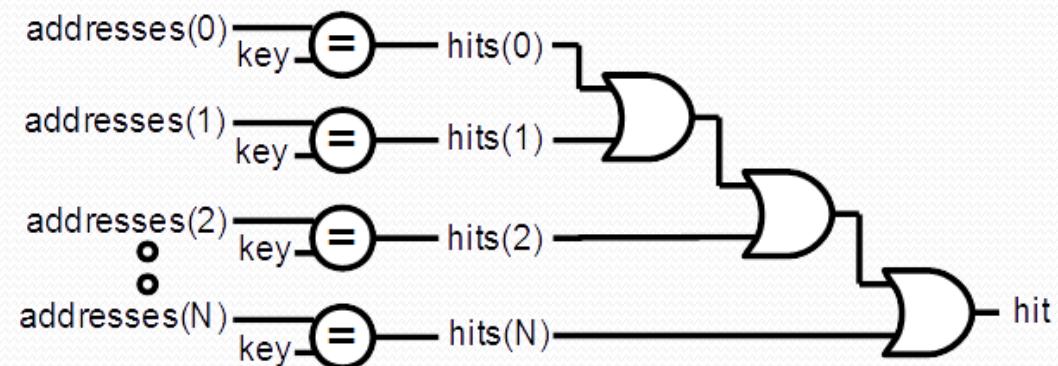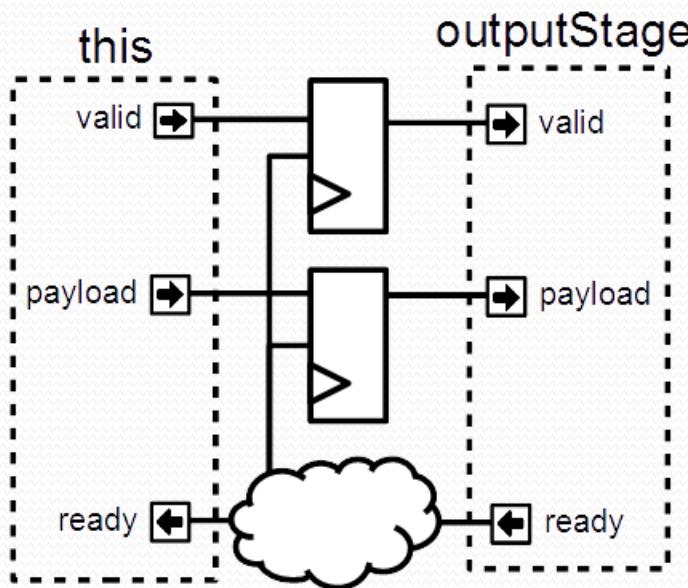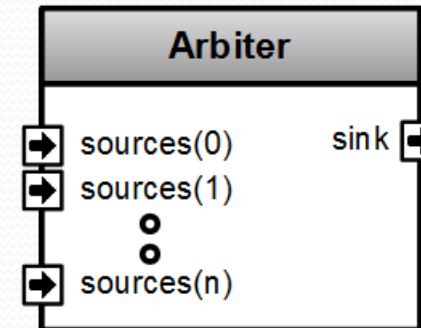

Basic abstractions

```
val timeout = Timeout(1000)
when(timeout){      //implicit conversion to Bool
    timeout.clear() //Clear the flag and the internal counter
}

//Create a counter of 10 states (0 to 9)
val counter = Counter(10)
counter.clear()        //When called it reset the counter. It's not a flag
counter.increment()   //When called it increment the counter. It's not a flag
counter.value         //current value
counter.valueNext    //Next value
counter.willOverflow //Flag that indicate if the counter overflow this cycle
when(counter === 5){ ...}
```

Flow, Stream


```
case class Flow[T <: Data](payloadType: T) extends Bundle {  
    val valid      = Bool  
    val payload : T = Flow(payloadType)  
}  
  
case class Stream[T <: Data](payloadType: T) extends Bundle {  
    val valid      = Bool  
    val ready      = Bool  
    val payload : T = Stream(payloadType)  
}  
  
val myStreamOfRGB= Stream(RGB(8,8,8))
```

Stream components

```
class Fifo[T <: Data](payloadType: T, depth: Int) extends Component {  
    val io = new Bundle {  
        val push = slave Stream (payloadType)  
        val pop  = master Stream (payloadType)  
    }  
    //...  
}
```



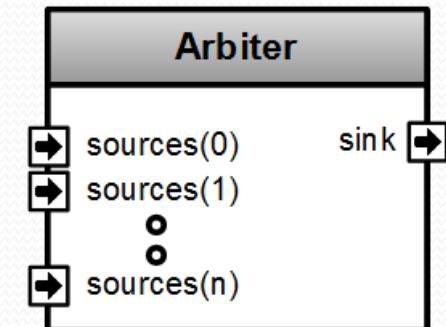
```
class Arbiter[T <: Data](payloadType: T, portCount: Int) extends Component {  
    val io = new Bundle {  
        val sources = Vec(slave(Stream(payloadType)), portCount)  
        val sink   = master(Stream(payloadType))  
    }  
    //...  
}
```



Stream functions


```
case class Stream[T <: Data](payloadType: T) extends Bundle {  
    // ...  
    def connectFrom(that: Stream[T]) = {  
        // some connections between this and that  
    }  
    def stage(): Stream[T] = {  
        val outputStage = Stream(dataType)  
        val validReg    = RegInit(False)  
        val payloadReg = Reg(payloadType)  
        // some logic  
        return outputStage  
    }  
    def << (that: Stream[T]) = this.connectFrom(that)  
    def <-< (that: Stream[T]) = this << that.stage()  
}
```
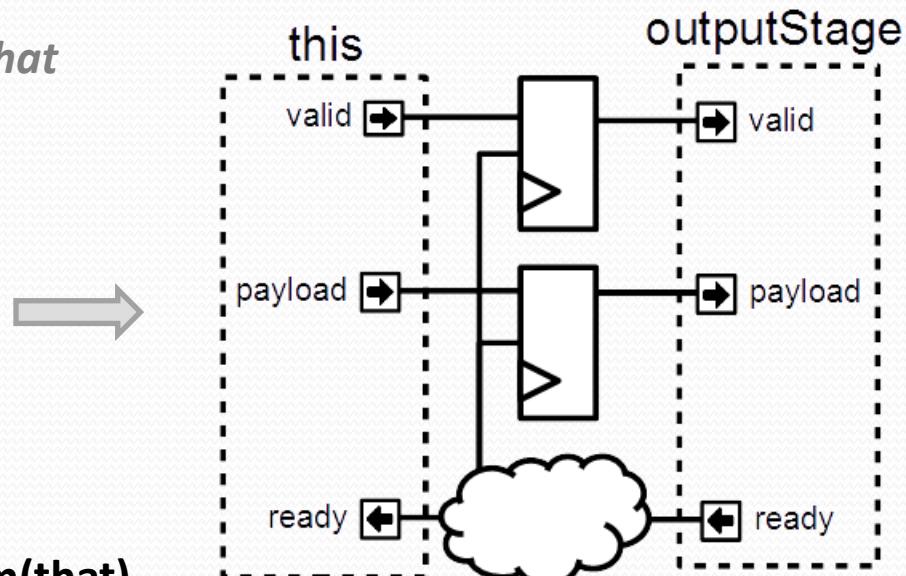
```
val myStreamA,myStreamB = Stream(UInt(8 bits))  
myStreamA <-< myStreamB
```



Functional programming

```
val addresses = Vec(UInt(8 bits),4)
val key = UInt(8 bits)
val hits = addresses.map(address => address === key)
val hit = hits.reduce((a,b) => a || b)
```

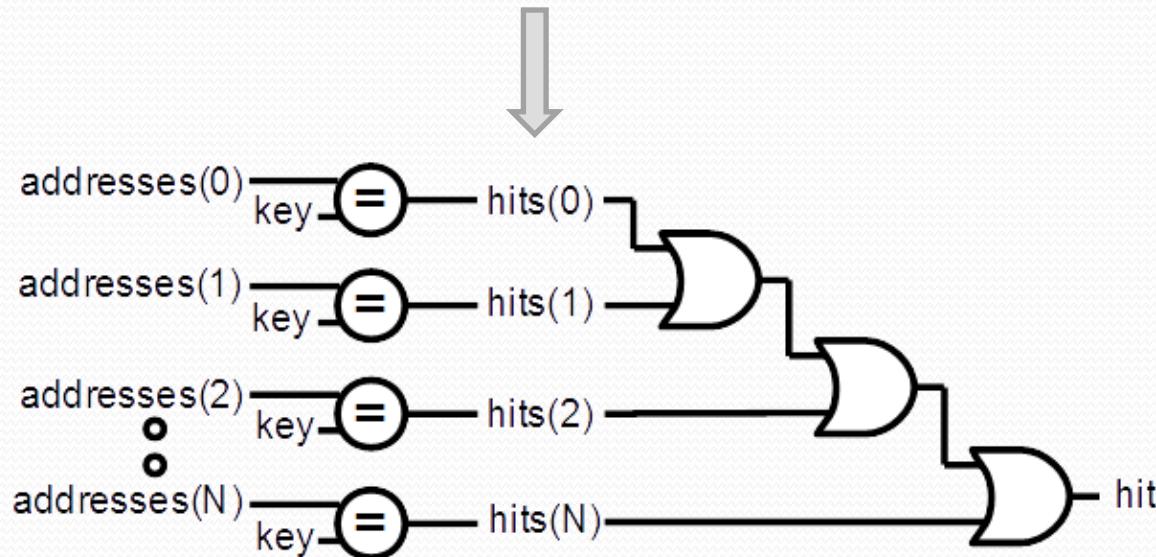

Scala is here to help you

```
class SinusGenerator(resolutionWidth : Int, sampleCount : Int) extends Component {  
    val io = new Bundle {  
        val sin = out SInt (resolutionWidth bits)  
    }  
  
    def sinTable = (0 until sampleCount).map(sampleIndex => {  
        val sinValue = Math.sin(2 * Math.PI * sampleIndex / sampleCount)  
        S((sinValue * ((1 << resolutionWidth) / 2 - 1)).toInt, resolutionWidth bits)  
    })  
  
    val rom    = Mem(SInt(resolutionWidth bits), initialContent = sinTable)  
    val phase  = CounterFreeRun(sampleCount)  
    io.sin := rom.readSync(phase)  
}
```



Netlist analyser / Latency analysis

```
class MyComponentWithLatencyAssert extends Component {
    val io = new Bundle {
        val slavePort = slave Stream (UInt(8 bits))
        val masterPort = master Stream (UInt(8 bits))
    }

    //These 3 line are equivalent to io.slavePort.queue(16) >/-> io.masterPort
    val fifo = new StreamFifo((UInt(8 bits)),16)
    fifo.io.push << io.slavePort      // << is a connection operator without decoupling
    fifo.io.pop >/-> io.masterPort //>/-> is a connection operator with decoupling

    assert(3 == latencyAnalysis(io.slavePort.payload,io.masterPort.payload))
    assert(2 == latencyAnalysis(io.masterPort.ready,io.slavePort.ready))
}
```

Meta-hardware description examples

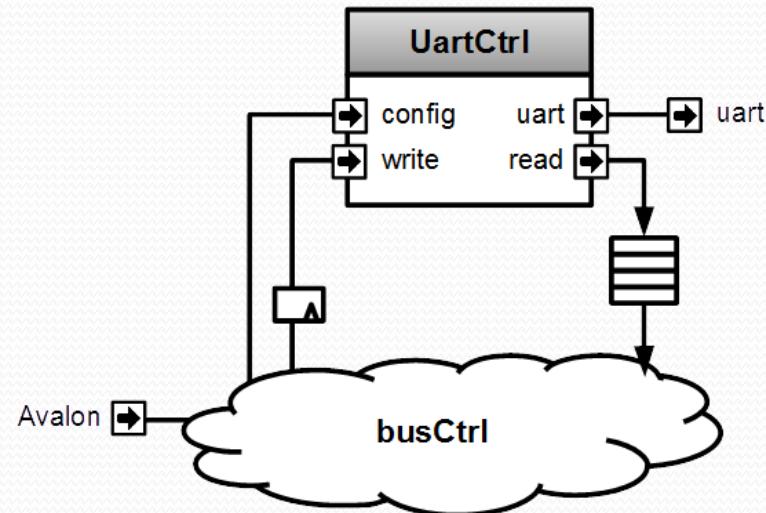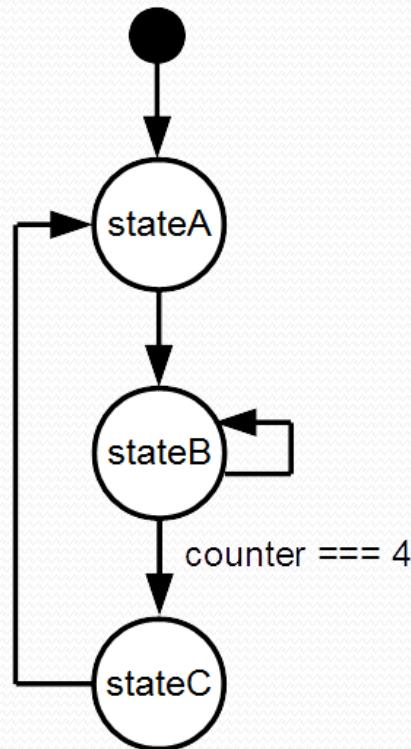


FSM

- They could be defined with regular syntax (Enum, Switch)
- You can also use a much more friendly syntax, fully integrated, with following features :
 - onEntry / onExit / whenIsActive / whenIsNext blocs
 - State with inner FSM
 - State with multiple inner FSM (parallel execution)
 - Delay state
 - You can extends the syntax by defining new state types

FSM style A
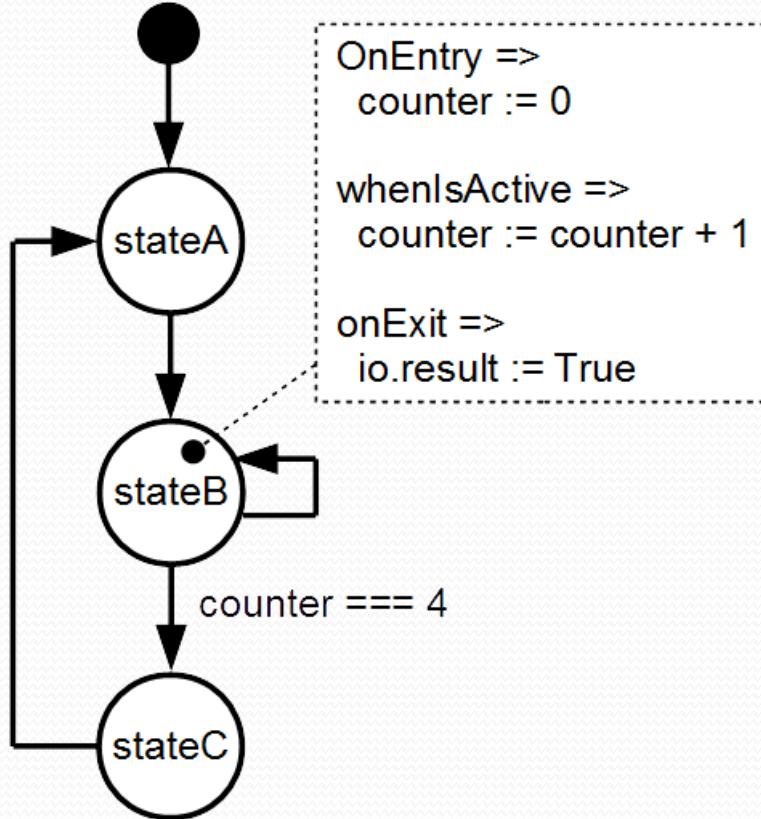
```
val io = new Bundle{
    val result = out Bool
}
```



```
val fsm = new StateMachine{
    io.result := False
    val counter = Reg(UInt(8 bits)) init (0)


    val stateA : State = new State with EntryPoint{
        whenIsActive (goto(stateB))
    }

    val stateB : State = new State{
        onEntry(counter := 0)
        whenIsActive {
            counter := counter + 1
            when(counter === 4){
                goto(stateC)
            }
        }
        onExit(io.result := True)
    }

    val stateC : State = new State{
        whenIsActive (goto(stateA))
    }
}
```

FSM style B
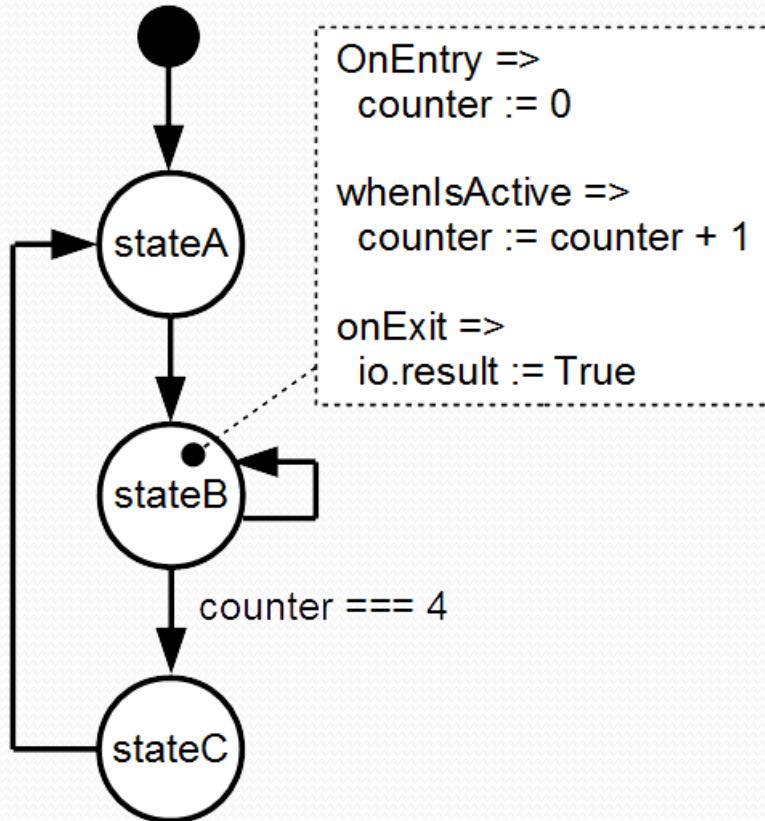
```
val io = new Bundle{
    val result = out Bool
}
```



```
val fsm = new StateMachine{
    val stateA = new State with EntryPoint
    val stateB = new State
    val stateC = new State
}
```


```
val counter = Reg(UInt(8 bits)) init (0)
io.result := False
```


```
stateA
    .whenIsActive (goto(stateB))
```

```
stateB
    .onEntry(counter := 0)
    .whenIsActive {
        counter := counter + 1
        when(counter === 4){
            goto(stateC)
        }
    }
    .onExit(io.result := True)
```

```
stateC
    .whenIsActive (goto(stateA))
}
```

Meta-hardware description

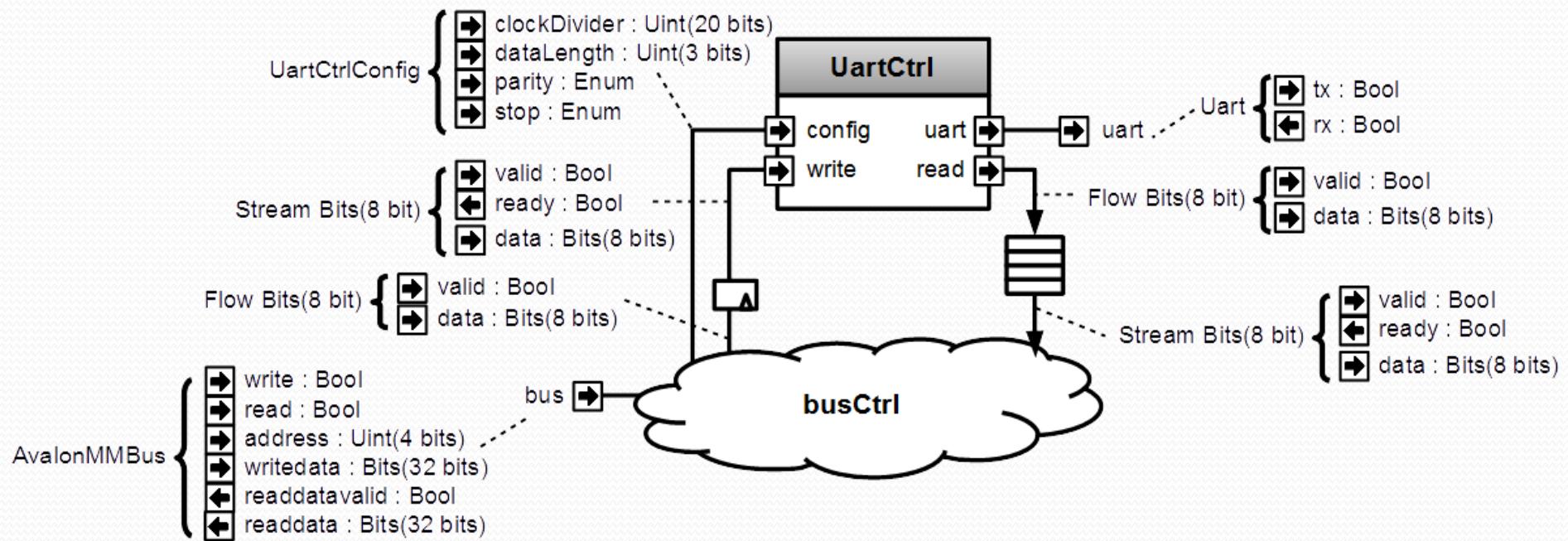

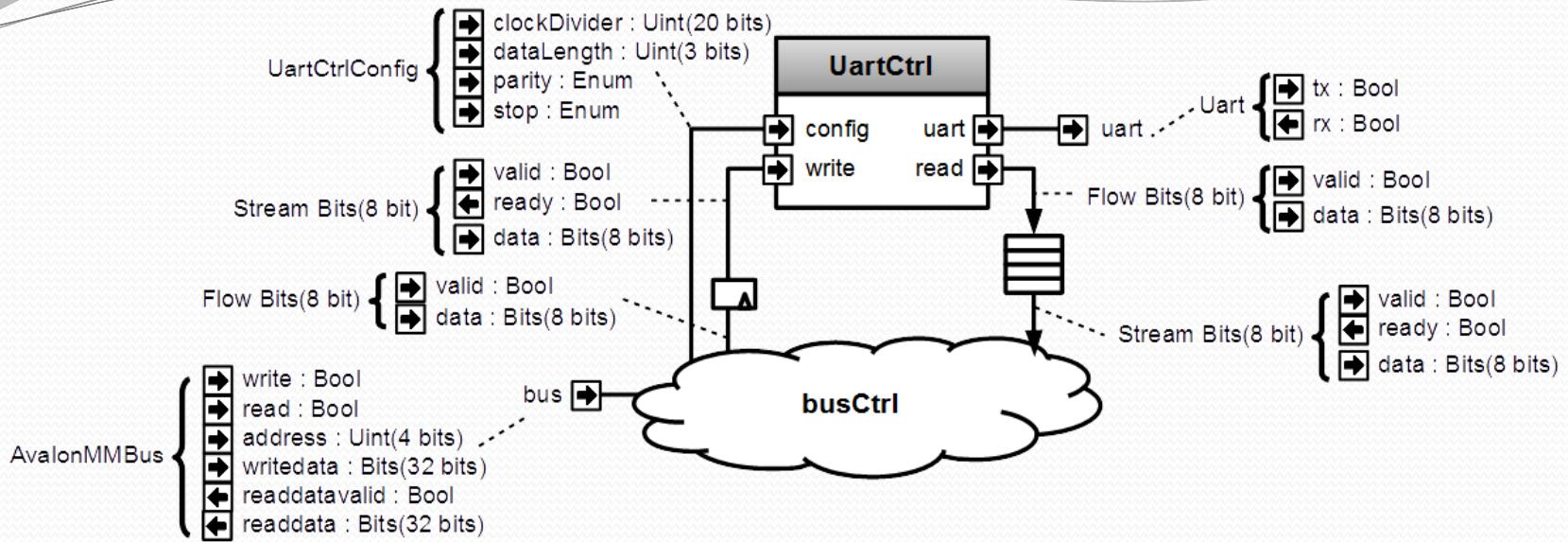

Name	Type	Access	Address	Description
clockDivider	UInt	RW	0	Set the UartCtrl clock divider
frame	UartCtrlFrameConfig	RW	4	Set the dataLength, the parity and the stop bit configuration
writeCmd	Bits	W	8	Send a write command to the UartCtrl
writeBusy	Bool	R	8	Bit 0 => zero when a new writeCmd could be sent
read	Bool / Bits	R	12	Bit 7 downto 0 => fifo pop payload Bit 31 => fifo pop valid

```

class AvalonUartCtrl(uartCtrlConfig : UartCtrlGenerics, rxFifoDepth : Int) extends Component{
    val io = new Bundle{
        val bus = slave(AvalonMM(...))
        val uart = master(Uart())
    }

    val uartCtrl = new UartCtrl(uartCtrlConfig)
    io.uart <> uartCtrl.io.uart

    val busCtrl = AvalonMMSlaveFactory(io.bus)

    //Make clockDivider register
    busCtrl.driveAndRead(uartCtrl.io.config.clockDivider, address = 0)

    //Make frame register
    busCtrl.driveAndRead(uartCtrl.io.config.frame, address = 4)

    //Make writeCmd register
    val writeFlow = busCtrl.createAndDriveFlow(Bits(uartCtrlConfig.dataWidthMax bits), address = 8)
    writeFlow.toStream.stage() >> uartCtrl.io.write

    //Make writeBusy register
    busCtrl.read(uartCtrl.io.write.valid, address = 8)

    //Make read register
    busCtrl.readStreamNonBlocking(uartCtrl.io.read.toStream.queue(rxFifoDepth),
                                address = 12, validBitOffset = 31, payloadBitOffset = 0)
}

```

About FSM and AvalonMMSlaveFactory

Both aren't part of Spinal core but are implemented on the top of it in the Spinal lib. Which mean these tools were created without any special interaction or special knowledge of the Spinal compiler.

They are only a mix of Scala OOP/FP with some Spinal basic syntax to generate the right hardware !

About Scala

- Free Scala IDE (eclipse, intelij)
 - Highlight syntax error
 - Renaming flexibility
 - Intelligent auto completion
 - Code's structure overview
 - Navigation tools
- Allow you to extend the language
- Provide many libraries

Spinal work perfectly on FPGA

- RISCV CPU, 5 stages, 1.15 DMIPS/Mhz
 - MUL/DIV
 - Instruction/Data cache
 - Interrupts
 - JTAG debugging
- Avalon/APB UART
- Avalon VGA
- Pipelined and multi-core fractal accelerator

About Spinal project

- Completely open source :
 - <https://github.com/SpinalHDL/SpinalHDL>
- Online documentation :
 - <https://spinalhdl.github.io/SpinalDoc/>
- Ready to use base project :
 - <https://github.com/SpinalHDL/SpinalBaseProject>
- Communication channels :
 - spinalhdl@gmail.com
 - <https://gitter.im/SpinalHDL/SpinalHDL>
 - <https://github.com/SpinalHDL/SpinalHDL/issues>